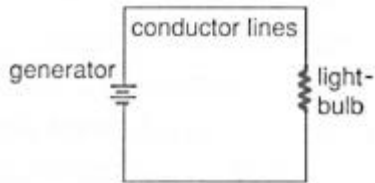


NETWORKS

Networks are based on electronic circuit, whose name derives from the latin word for a circle or loop. As you probably already know, the simplest form of circuit consists of a generator, line and resistor, such as a battery, wire and lightbulb. The schematic representation of this is as follows:




OHM'S LAW

All components of a circuit are described by a simple principle known as Ohm's Law. It simply states that voltage across a resistor equals the current through it times a quantity known as resistance.

$$V = IR$$

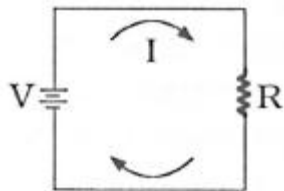Voltage is measured in volts (V), current in amps (A) and resistance in ohms (Ω). (These units are named after the scientists Volta, Ampere and Ohm)




KIRCHOFF'S LAW

Voltage:

The total voltage in a circuit must add up to zero. This means that voltage at the source must be equal to the total voltage drop across the resistors in a circuit. Ohm's law ($V=IR$) also governs the magnitude of the voltage drop across each resistive element in a circuit. (note: short wires also have a resistance, however, this is insignificant compared to the R of a resistor – we will address long wires later)

Current:

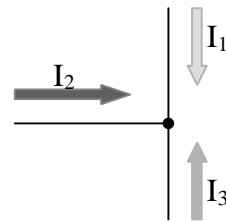The sum of the currents flowing to any one point in a circuit, known as a node, must be zero.



$$I_1 + I_2 + I_3 = 0$$


This means that if I_1 is +1 amp, and I_2 is +2 amps then I_3 must be -3 amps (in other words, I_3 is 3 amps flowing away from the node)

DETERMINING RESISTANCE

If you have more than one resistor in a circuit, they can be combined into a single equivalent resistance, R_T . The method for combining depends on whether resistors are in series or in parallel.

NETWORKS


If resistors are in *series*:

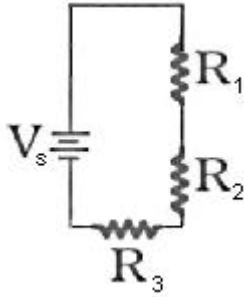

$$R_{\text{Total}} = R_1 + R_2 + R_3$$

Current, I , is the same through each resistor, and equal to: $I = V_{\text{Source}}/R_{\text{Total}}$

If resistors are wired in *parallel*:

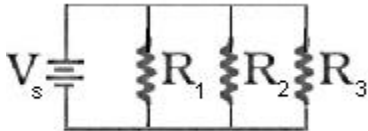


$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3$$

Voltage, V , is the same across each resistor and equal to V_s .

If you have a combination, convert the parallel portion of the circuit to one resistance, and then add the resistors as if they were in series.


EXAMPLE

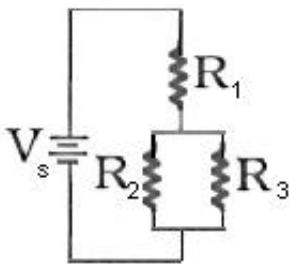

$$V_{\text{Source}} = 12\text{V}$$

$$R_1 = 1000\Omega \quad R_2 = 400\Omega \quad R_3 = 400\Omega$$

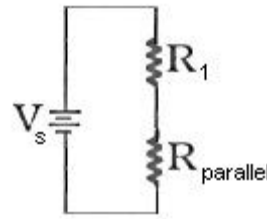First convert R_2 and R_3 to a single resistance, R_{parallel} .



$$1/R_{\text{parallel}} = 1/R_2 + 1/R_3$$

$$1/R_{\text{parallel}} = 1/400\Omega + 1/400\Omega$$

$$1/R_{\text{parallel}} = 2/400\Omega$$

$$R_{\text{parallel}} = 200\Omega$$

Now add R_1 and R_{parallel} .

$$R_1 + R_{\text{parallel}} = R_{\text{Total}}$$

$$1000\Omega + 200\Omega = 1200\Omega$$

Use R_{Total} to determine the current through the loop:

$$V_{\text{Source}} = I_{\text{Total}} R_{\text{Total}}$$

$$12\text{V} = I_{\text{Total}} \times 1200\Omega$$

$$I_{\text{Total}} = .01 \text{ A}$$

Because R_1 and R_{parallel} were in series, this is the current that passes through each of them. To find the voltage through each resistor, use Ohm's Law:

$$V_1 = I_{\text{Total}} R_1$$

$$V_1 = .01 \text{ A} \times 1000\Omega$$

$$V_1 = 10\text{V}$$

$$V_{\text{parallel}} = I_{\text{Total}} R_{\text{parallel}}$$

$$V_{\text{parallel}} = .01 \text{ A} \times 200\Omega$$

$$V_{\text{parallel}} = 2\text{V}$$

notice that the voltage drops add up to $12\text{V} = V_{\text{Source}}$.

To find the current through and voltage across R_2 and R_3 you must use what you know about the voltage, V_{parallel} , across the two of them. Because they are wired in parallel, the voltage across each of them is the same. It is also equal to V_{parallel} .

$$V_2 = V_3 = V_{\text{parallel}}$$

$$V_2 = 2\text{V}$$

$$V_3 = 2\text{V}$$

To find the current through each, again use Ohm's law:

$$V_2 = I_2 R_2$$


$$2V = I_2 \times 400\Omega$$

$$I_2 = .005 \text{ A}$$

$$V_3 = I_3 R_3$$

$$2V = I_3 \times 400\Omega$$

$$I_3 = .005 \text{ A}$$

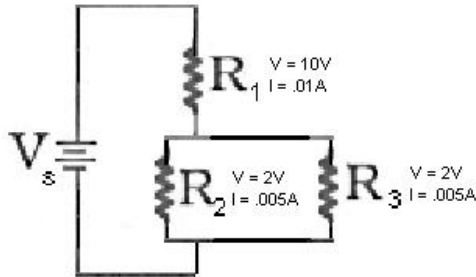

Resistance of a device can be a function of different properties, such as temperature. In a wire resistance is dependent upon the material used, the length of the wire, and its cross-sectional area:

Resistance = resistivity of the material \times length of wire / cross-sectional area of the wire

$$R = \rho L/A$$

JOULE'S LAW

Another important equation relating to all circuits is Joule's Law. It states:

Power in a component (measured in watts) = Current through it times the voltage across it

$$P = VI$$

And, knowing that $V = IR$, we can substitute to create another relationship:

$$P = I \times (IR)$$

$$P = I^2R$$

From this, one is able to determine power losses due to resistance at different current levels.

Thomas Edison worked with these equations to help him develop his vision of a great New York network of electricity.

ELECTROMAGNETISM

Faraday observed that when current flows through a wire that is in a magnetic field, this wire experiences a force in a direction perpendicular to both the magnetic field and the current flow. The magnitude of the force on this wire is:

$$F = iLB$$

Where F is the force on the wire, i is the current running through the wire, L is the length of wire that is in the magnetic field, and B is the magnetic field strength.

This observation serves as the fundamental basis for many electromagnetic devices including motors, loudspeakers and electromagnetic meters.

