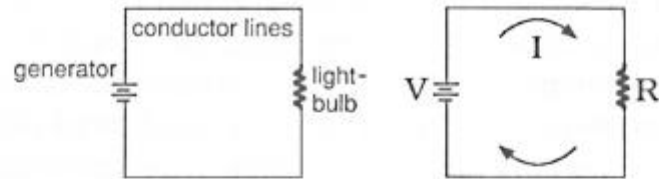


## Networks for Electric Lighting



### Ohm's law (1)

$$\begin{array}{ccccc} V & = & I & R \\ \text{voltage} & & \text{current} & \text{resistance} \\ \text{at the} & & \text{flowing} & \text{of the} \\ \text{generator} & & \text{in the} & \text{lamp} \\ \text{volts} & & \text{circuit} & \\ & & \text{amps} & \text{ohms} \end{array}$$

### Joule's law (2)

$$\begin{array}{ccccc} P & = & V & I \\ \text{power} & & \text{voltage} & \text{current} \\ \text{from} & & \text{at the} & \text{flowing} \\ \text{the} & & \text{generator} & \text{in the} \\ \text{generator} & & & \text{circuit} \\ \text{watts} & & \text{volts} & \text{amps} \end{array}$$

### Substitute (1) into (2)

$$\begin{array}{ccccc} I^2 & R & = & P \\ \text{current} & \text{resistance} & & \text{power} \\ \text{squared} & \text{of the} & & \text{converted} \\ & \text{lamp} & & \text{to} \\ & & & \text{light} \end{array}$$

Note: Formulas for this simplified network neglect the power losses in the lines.

## Current in One Coil

**Ohm's law,  $V = IR$**       **Resistance  $R = \rho \frac{L}{A}$**

$V =$  *The voltage* produced by the battery which we assume, for Henry's experiment 15, to have been 1 volt.

$R =$  *The resistance* throughout each of the 9 circuits of length  $L$ .

$L = 60$  ft., *the length* for one wire going from the battery to the magnet, coiled around the iron core, and returning to the battery (one circuit).

$A = 0.00159$  sq. in. the *cross-sectional* area of the .045-in. diameter copper wire.

$\rho =$  *The resistivity* of the wire material, which for copper is  $0.67 \times 10^{-6}$  ohm-in.


Hence, the resistance in each of the 9 parallel circuits is

$$R = 0.67 \times 10^{-6} \frac{60 \times 12}{1590 \times 10^{-6}} = 0.303 \text{ ohms}$$

and, from Ohm's law, we calculate the current as

$$I = \frac{V}{R} = \frac{1}{0.303} = 3.3 \text{ amps in each of 9 parallel circuits.}$$

## Series Circuit for 9 Coils

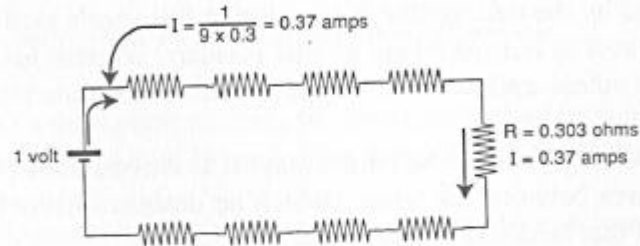

$$I = \frac{V}{R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7 + R_8 + R_9} = \frac{1}{9 \times 0.303} = 0.37 \text{ amps}$$


$$\frac{IN}{L_c} = \frac{0.37(9 \times 80)}{23} = \frac{266}{23} = 11.6 \frac{\text{ampere-turns}}{\text{in.}}; \quad B \approx 30,000 \frac{\text{lines of flux}^*}{\text{sq. in.}}$$

$$2F = \frac{2(30,000)^2 4}{7.213 \times 10^7} = 100 \text{ lbs.}$$

Henry got over seven times the strength by using a parallel instead of a series circuit for his electromagnet.

\*Note that  $B$  is not linearly proportional to  $\frac{IN}{L_c}$ .

## Parallel Circuit for 9 Coils

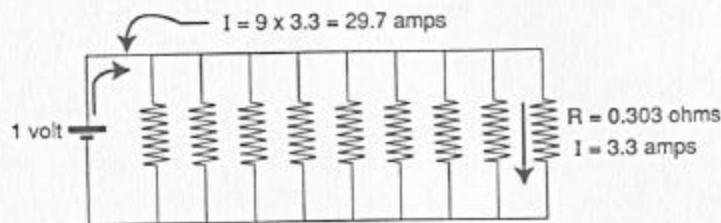


$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} + \frac{V}{R_4} + \frac{V}{R_5} + \frac{V}{R_6} + \frac{V}{R_7} + \frac{V}{R_8} + \frac{V}{R_9} = 9 \times \frac{1}{0.303} = 29.7 \text{ amps}$$

$$\frac{IN}{L_c} = \frac{(3.3)(720)}{23} = 103 \frac{\text{ampere-turns}}{\text{in.}} \quad B \approx 82,000 \frac{\text{lines of flux}}{\text{sq. in.}}$$

$$2F = \frac{2(82,000)^2 4}{7.213 \times 10^7} = 746 \text{ lbs.}$$

# Joseph Henry's Magnet

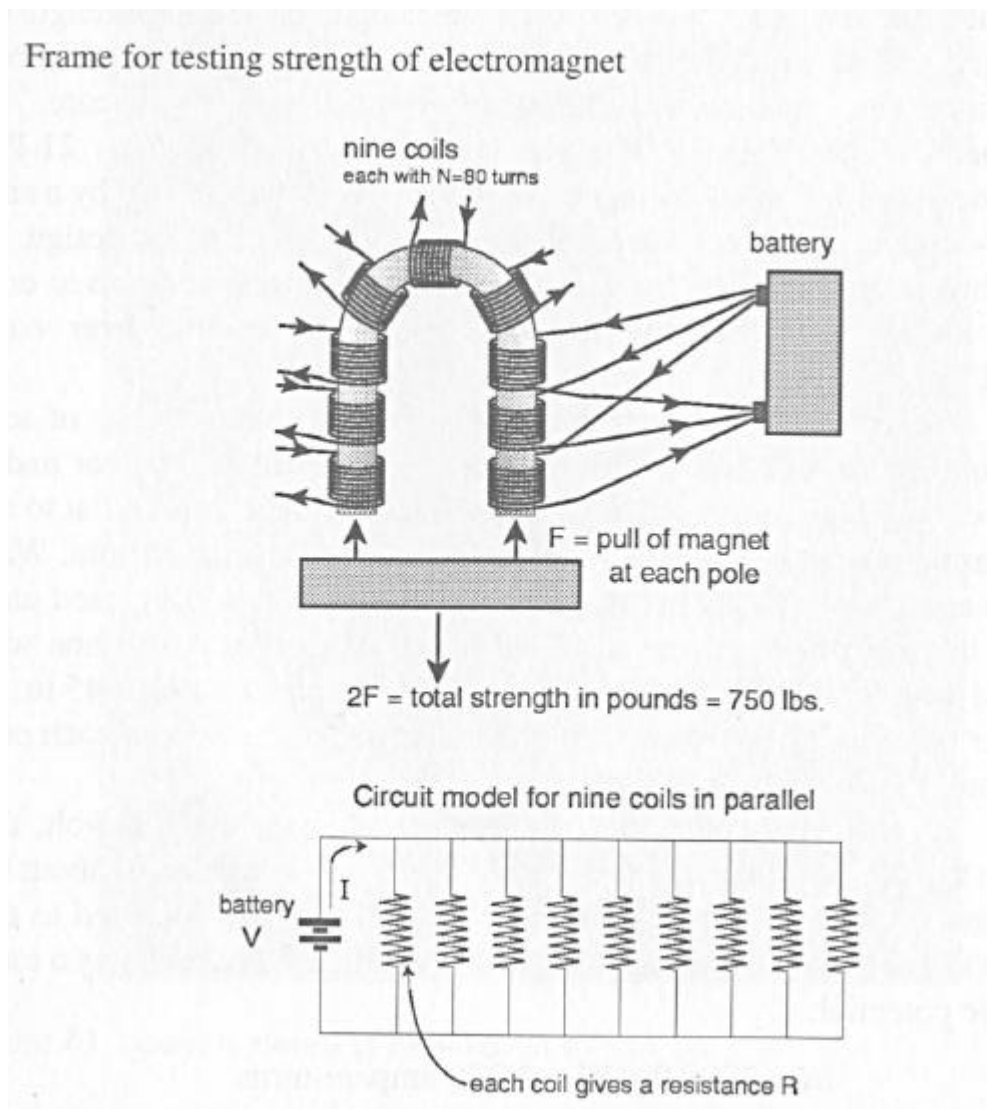

## Magnet Strength

The strength of the electromagnet,  $F$ , depends upon the flux density  $B$  and the pole area  $A$ .

$$F = \frac{B^2 A}{72,130,000} \text{ lbs.}$$

The flux density  $B$  depends upon the number of turns of wire ( $N = 9 \times 80 = 720$  turns) coiled around a core of length  $L_C = 23$  in., the current flowing through the wires ( $I = 3.3$  amps in each turn) and the material properties of the core:

$$\frac{IN}{L_C} = \frac{3.3(720)}{23} = 103 \text{ ampere-turns per in.}$$

The flux density varies with the quantity  $IN/L_C$  as well as with the materials; it must be taken from experimentally derived magnetization curves. For the soft iron used by Henry, we can estimate, taking standard curves for iron and steel with  $IN/L_C = 103$ ,

$$B = 82,000 \text{ lines of flux per sq. in.}^*$$

The pole area  $A$  is the cross-sectioned area of one end of the horseshoe core or  $2 \times 2 = 4$  sq. in. Therefore, the total strength of both poles

$$2F = \frac{2(82,000)^2(4)}{7.213 \times 10^7} = 746 \text{ lbs.}$$

is about what Henry measured.

\*For such curves see, for example A. L. Cook and C. C. Carr, *Elements of Electrical Engineering*, 5th ed., New York, 1947, p. 30. We have interpolated and picked the value that gives Henry's result.